

How to fit transmission lines with ZFit

I Introduction

ZFit is the impedance fitting tool of EC-Lab[®]. This note will describe how to fit transmission lines using one equivalent circuit elements contained in ZFit.

It is well known that the Warburg impedance is equivalent to that of a semi-infinite large network *i.e.* a transmission line, as shown in Fig. 1 [1, 2]. Moreover, the transmission lines are often used for modeling porous electrodes, for example in the field of photovoltaics.

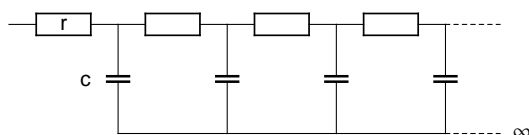


Fig. 1: The equivalent circuit of the Warburg impedance.

More recently it has been shown [3] that the impedance of a L-long transmission line made of χ and ζ elements and terminated by a Z_L element (Fig. 2) is given by the general expression:

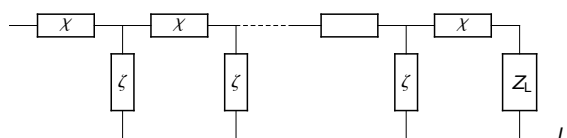


Fig. 2: Uniform transmission line made of χ and ζ elements and terminated by Z_L [3].

$$Z = \frac{(\zeta \chi - Z_L^2) \operatorname{sh} \left(\frac{L\sqrt{\chi}}{\sqrt{\zeta}} \right)}{Z_L \operatorname{sh} \left(\frac{L\sqrt{\chi}}{\sqrt{\zeta}} \right) + \sqrt{\zeta \chi} \operatorname{ch} \left(\frac{L\sqrt{\chi}}{\sqrt{\zeta}} \right)} + Z_L$$

¹The transmission lines are named according to the U- $\chi\zeta$ format where U means uniform distributed and χ and ζ are the element of the transmission line.

with three limiting cases

- open-circuited transmission line

$$Z_L = \infty \Rightarrow Z = \sqrt{\zeta \chi} \operatorname{coth} \left(\frac{L\sqrt{\chi}}{\sqrt{\zeta}} \right) \quad (1)$$

- short-circuited transmission line

$$Z_L = 0 \Rightarrow Z = \sqrt{\zeta \chi} \operatorname{th} \left(\frac{L\sqrt{\chi}}{\sqrt{\zeta}} \right) \quad (2)$$

- semi-infinite transmission line

$$L \rightarrow \infty \Rightarrow Z = \sqrt{\zeta \chi} \quad (3)$$

Hereafter, some transmission lines are described and the corresponding "simple" equivalent circuit elements are shown. The open-circuited transmission lines will be explained, followed by short-circuited and semi-infinite transmission lines.

II Open-circuited transmission lines $Z_L = \infty$

II.1 Open-circuited URC (Uniform distributed RC)

Let us consider the open-circuited transmission line made of r and c elements (Fig. 3).

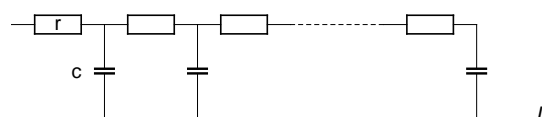


Fig. 3: L-long open uniform distributed RC (URC) transmission line [4, 5].

Using Eq. (1), the impedance of the URC transmission line is given by ⁽¹⁾

$$\chi = r, \zeta = \frac{1}{j\omega c} \Rightarrow Z = \sqrt{r} \frac{\operatorname{coth}(L\sqrt{rcj\omega})}{\sqrt{cj\omega}}$$

with $\omega = 2\pi f$. This impedance is similar to that of the M element of ZFit

$$Z_M = R_d \frac{\coth \sqrt{\tau_d j \omega}}{\sqrt{\tau_d j \omega}}, R_d = Lr, \tau_d = L^2 r c$$

II.2 Open-circuited URQ

Replacing c elements by q elements, with $Z_q = 1/(q(j\omega)^\alpha)$, leads to transmission line shown in Fig. 4.

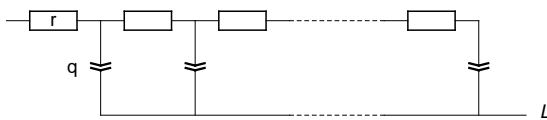


Fig. 4: L-long open uniform distributed RQ (URQ) transmission line.

The transmission line impedance is given by

$$\chi = r, \zeta = \frac{1}{q(j\omega)^\alpha} \Rightarrow Z = \sqrt{r} \frac{\coth(L\sqrt{r q}(j\omega)^{\alpha/2})}{\sqrt{q}(j\omega)^{\alpha/2}}$$

This impedance is similar to that of the M_a element of ZFit

$$Z_{M_a} = R \frac{\coth(\tau j \omega)^{\alpha/2}}{(\tau j \omega)^{\alpha/2}} \text{ with } R = Lr, \tau = (L^2 r q)^{1/\alpha}$$

As an example a Nyquist impedance diagram of a battery Ni-MH 1900 mAh is shown in Fig. 5. The equivalent circuit $R1+L1+Q1/(R2+Ma3)$, containing a M_a element, is chosen to fit the data shown in Fig. 5. The values of the parameters, obtained using the ZFit tool of ECLab, are $R1 = 0.049 \Omega$, $L1 = 0.154 \times 10^{-6} \text{ H}$, $Q1 = 0.66 \text{ F s}^{\alpha-1}$, $\alpha1 = 0.61$, $R2 = 0.0236 \Omega$, $R3 = Lr = 0.057 \Omega$, $\tau3 = (L^2 r q)^{1/\alpha} = 2.25 \text{ s}$ and $\alpha3 = 0.89$.

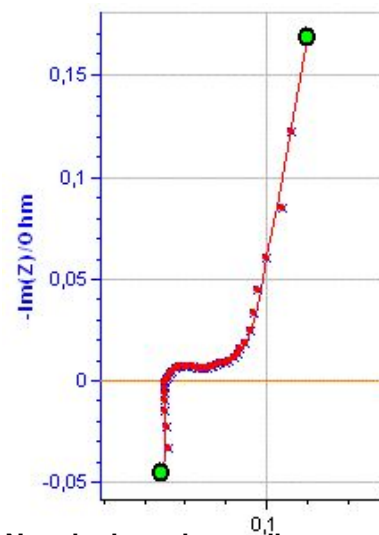


Fig. 5: Nyquist impedance diagram of a battery Ni-MH 1900 mAh.

II.3 Open-circuited UQC

The equivalent circuit of the so-called anomalous diffusion is shown in Fig. 6 [6].

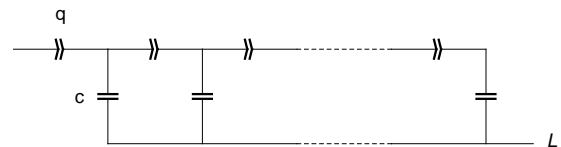


Fig. 6: L-long open uniform distributed QC (UQC) transmission line. Anomalous diffusion [6].

The anomalous diffusion impedance is given by

$$\chi = \frac{1}{q(j\omega)^\alpha}, \zeta = \frac{1}{c j \omega} \Rightarrow Z = \frac{\coth\left(L\sqrt{\frac{c}{q}}(j\omega)^{\frac{1}{2}-\frac{\alpha}{2}}\right)}{\sqrt{c q}(j\omega)^{\frac{\alpha}{2}+\frac{1}{2}}}$$

This impedance is similar to that of the M_g element of ZFit

$$Z_{M_g} = R \frac{\coth(\tau j \omega)^{\gamma/2}}{(\tau j \omega)^{1-\gamma/2}} \text{ with } \gamma = 1 - \alpha, R = c^{\frac{1}{\gamma}-1} L^{\frac{2}{\gamma}-1} q^{-1/\gamma}, \tau = c^{\frac{1}{\gamma}} L^2/\gamma q^{-1/\gamma}$$

III Short-circuited transmission lines $Z_L = 0$

III.1 Short-circuited URC



Fig. 7: L-long short-circuited uniform distributed RC (URC) transmission line.

Using Eq. (2), the impedance of the short-circuited transmission line made of r and c elements (Fig. 7) is given by

$$\chi = r, \zeta = \frac{1}{c j \omega} \Rightarrow Z = r \frac{\text{th}(L \sqrt{r c j \omega})}{\sqrt{r c j \omega}} \quad (4)$$

This impedance is similar to that of the W_d element of ZFit

$$Z_{W_d} = R_d \frac{\text{th} \sqrt{\tau_d j \omega}}{\sqrt{\tau_d j \omega}}, R_d = L r, \tau_d = L^2 r c$$

IV Semi-infinite transmission lines $L \rightarrow \infty$

IV.1 Semi-infinite URC

The impedance of the semi-infinite transmission line shown in Fig. 1 is obtained making $L \rightarrow \infty$ in Eq. (4).

$$L \rightarrow \infty \Rightarrow Z = r \frac{\text{th}(L \sqrt{r c j \omega})}{\sqrt{r c j \omega}} \approx \frac{\sqrt{r}}{\sqrt{c j \omega}}$$

This expression is similar to that of the Warburg (W) element of ZFit

$$Z_W = \frac{2 \sigma}{\sqrt{j \omega}} \text{ with } \sigma = \frac{\sqrt{r}}{2 \sqrt{c}}$$

As an example a Nyquist impedance diagram of a Fe(II)/Fe(III) system is shown in Fig. 8.

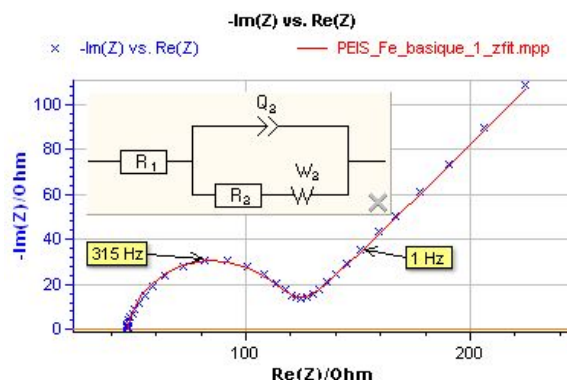


Fig. 8: Nyquist impedance diagram of a Fe(II)/Fe(III) system in basic medium.

The Randles circuit $R_1 + Q_2 / (R_2 + W_2)$, containing a Warburg element, is chosen to fit the data shown in Fig. 8. The values of the parameters for equivalent circuit are $R_1 = 47.57 \Omega$, $Q_2 = 17.09 \times 10^{-6} \text{ F s}^{\alpha-1}$, $\alpha = 0.885$, $R_2 = 70.94 \Omega$ and $\sigma_2 = 85.33 \Omega \text{ s}^{-1/2} \Rightarrow \sqrt{r/c} = 42.7 \Omega \text{ s}^{-1/2}$.

IV.2 Semi-infinite URRC

First of all, let us calculate the impedance of the L-long URRC transmission line (Fig. 9) corresponding to diffusion-reaction and diffusion-trapping impedance [7]:

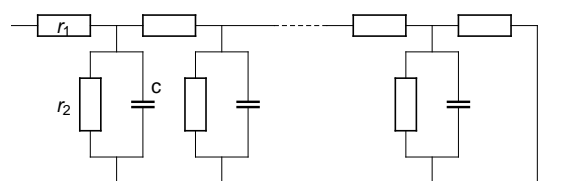


Fig. 9: L-long short-circuited uniform distributed RRC (URRC) transmission line.

$$\chi = r_1, \zeta = \frac{r_2}{1 + r_2 c j \omega} \Rightarrow$$

$$Z = \frac{\text{th} \left(L \sqrt{\frac{r_1}{r_2} (1 + r_2 c j \omega)} \right)}{\sqrt{r_1 r_2} \sqrt{1 + r_2 c j \omega}}$$

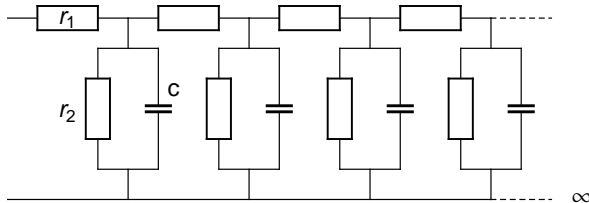


Fig. 10: Semi-infinite short-circuited uniform distributed RRC (URRC) transmission line.

With $L \rightarrow \infty$ it is obtained [8]:

$$L \rightarrow \infty \Rightarrow Z \approx \frac{\sqrt{r_1 r_2}}{\sqrt{1 + r_2 c j \omega}}$$

This expression is similar to that of the Gerischer element G of ZFit [9]:

$$Z_G = \frac{R_G}{\sqrt{1 + \tau_G j \omega}}, R_G = \sqrt{r_1 r_2}, \tau_G = r_2 c$$

IV.3 Semi-infinite URRQ

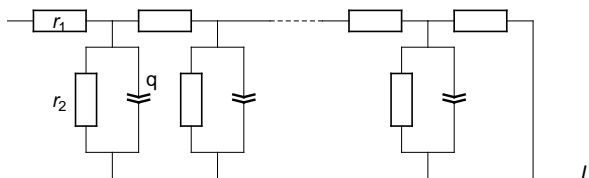


Fig. 11: L-long short-circuited uniform distributed RRQ (URRQ) transmission line.

Replacing c elements by q elements

$$\chi = r_1, \zeta = \frac{r_2}{1 + r_2 q (j \omega)^\alpha} \Rightarrow Z = \frac{\text{th} \left(L \sqrt{\frac{r_1}{r_2} (1 + r_2 q (j \omega)^\alpha)} \right)}{\sqrt{r_1 r_2} \sqrt{1 + r_2 q (j \omega)^\alpha}}$$

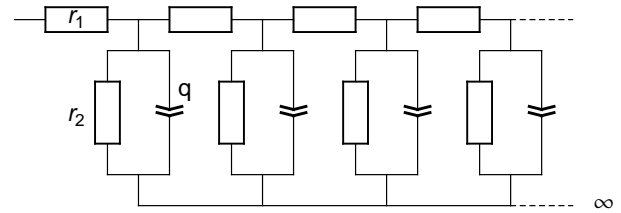


Fig. 12: Semi-infinite short-circuited uniform distributed RRQ (URRQ) transmission line.

and

$$L \rightarrow \infty \Rightarrow Z \approx \frac{\sqrt{r_1 r_2}}{\sqrt{1 + r_2 q (j \omega)^\alpha}}$$

This expression is similar to that of the G_a element of ZFit

$$Z_{G_a} = \frac{R}{\sqrt{1 + \tau (j \omega)^\alpha}}, R = \sqrt{r_1 r_2}, \tau = r_2 q$$

V Conclusion

Seven elements, W, Wd, M, Ma, Mg, G and G_a , available in ZFit, can be used to represent the impedance of seven different transmission lines, as summarized in the table below (Tabs. 1 (p. 4), 2 (p. 6)).

Table 1: Summary table.







Transmission line	ZFit Element	
Open Circuited	URC	M
	URQ	Ma
	UQC	Mg
Short circuited	URC	Wd
	URQ	W
Semi- ∞	URRC	G
	URRQ	G_a

References

- [1] J. C. WANG, *J. Electrochem. Soc.* **134**, 1915 (1987).
- [2] M. SLUYTERS-REHBACH, *Pure & Appl. Chem.* **66**, 1831 (1994).
- [3] J. BISQUERT, *Phys. Chem. Chem. Phys.* **2**, 4185 (2000).
- [4] G. C. TEMES and J. W. LAPATRA, *Introduction to Circuits Synthesis and Design*, McGraw-Hill, New-York, 1977.
- [5] J.-P. DIARD, B. LE GORREC, and C. MONTELLA, *J. Electroanal. Chem.* **471**, 126 (1999).
- [6] J. BISQUERT and A. COMPTE, *J. Electroanal. Chem.* **499**, 112 (2001).
- [7] J.-P. DIARD and C. MONTELLA, *J. Electroanal. Chem.* **557**, 19 (2003).
- [8] B. A. BOUKAMP and H. J.-M. BOUWMEESTER, *Solid State Ionics* **157**, 29 (2003).
- [9] H. GERISCHER, *Z. Physik. Chem. (Leipzig)* **198**, 286 (1951).

Nicolas Murer, Ph. D.,
Aymeric Pellissier, Ph. D.,
Jean-Paul Diard, Pr.

Table 2: ZFit elements vs. transmission lines.

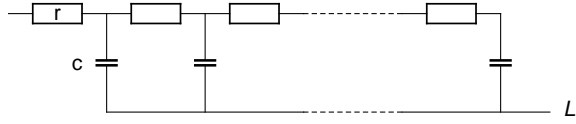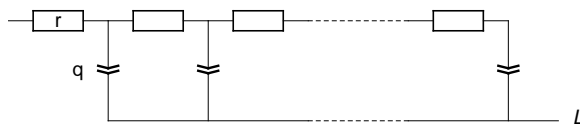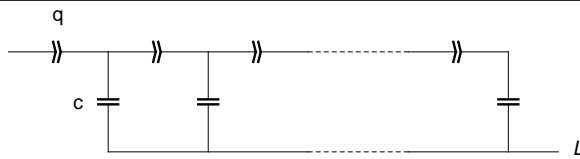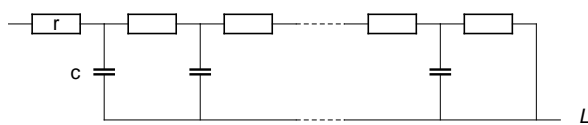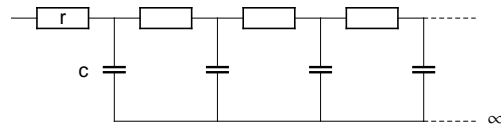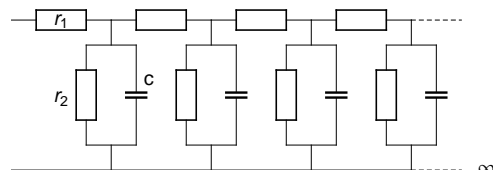ZFit element	Equations	Transmission line
M	$R_d \frac{\coth \sqrt{\tau_d j \omega}}{\sqrt{\tau_d j \omega}}$ $R_d = L r, \tau_d = L^2 r c$	
M _a	$R \frac{\coth(\tau j \omega)^{\alpha/2}}{(\tau j \omega)^{\alpha/2}}$ $R = L r$ $\tau = (L^2 r q)^{1/\alpha}$	
M _g	$R \frac{\coth(\tau j \omega)^{\gamma/2}}{(\tau j \omega)^{1-\gamma/2}}$ $R = c^{\frac{1}{\gamma}-1} L^{\frac{2}{\gamma}-1} q^{-1/\gamma}$ $\tau = c^{\frac{1}{\gamma}} L^{2/\gamma} q^{-1/\gamma}$	
W _d	$R_d \frac{\text{th} \sqrt{\tau_d j \omega}}{\sqrt{\tau_d j \omega}}$ $R_d = L r$ $\tau_d = L^2 r c$	
W	$\frac{2 \sigma}{\sqrt{j \omega}}$ $\sigma = \frac{\sqrt{r}}{2 \sqrt{c}}$	
G	$\frac{R_G}{\sqrt{1 + \tau_G j \omega}}$ $R_G = \sqrt{r_1 r_2}$ $\tau_G = r_2 c$	
G _a	$\frac{R_G}{\sqrt{1 + \tau_G (j \omega)^\alpha}}$ $R_G = \sqrt{r_1 r_2}$ $\tau_G = r_2 q$	